
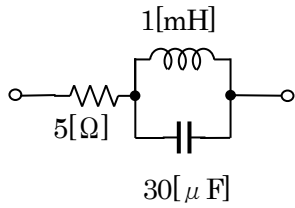


問1 次の回路の合成インピーダンスを求めよ。なお、周波数は1[KHz]とする。


(1)

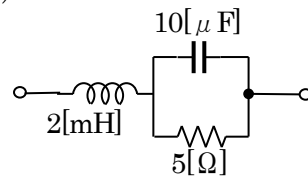


(2)




(3)

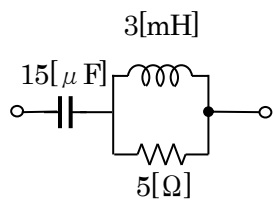

(4)

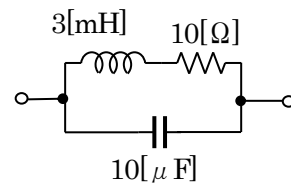

(5)

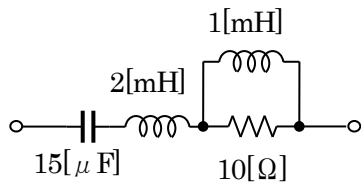

(6)

